

## 8-Bit ALU

By Phanuruj Sotthidat 64011544

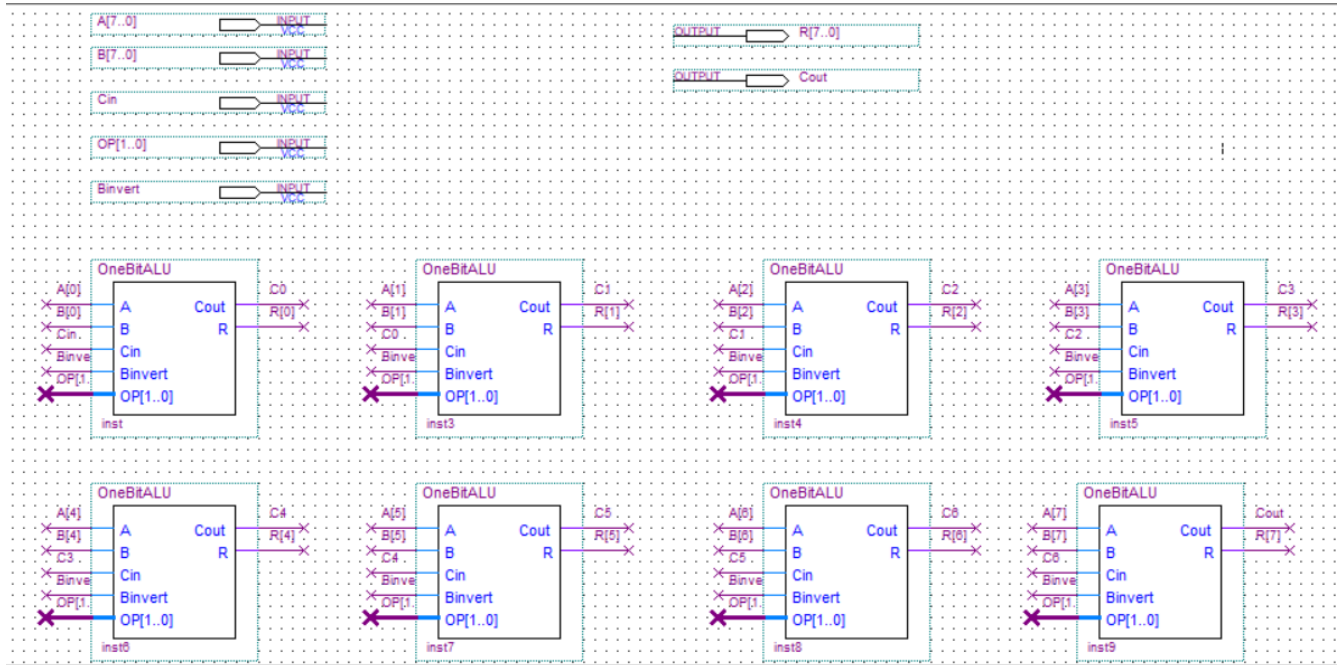


Figure 1: 8-bit ALU whole design.

This is my design for 8-bit ALU containing 8 of One-bit ALU which each One-bit ALU is connected by Cout and Cin for example; from Figure 2 shown below, in the left circuit Cout is C1 and the right circuit Cin is C1 which means that these two circuits connected by this Cout and Cin.

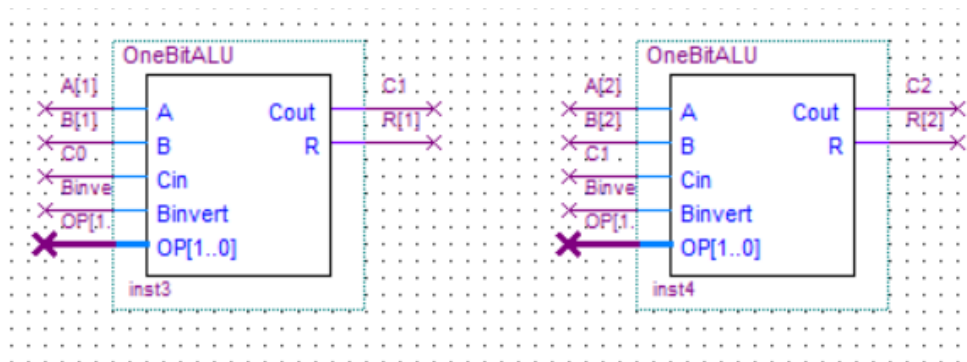


Figure 2: Circuit Connection.

For the inputs there are:

- Input(binary) **A[7..0]** from 0 to 7 which is each index corresponds to each digit.
- Input(binary) **B[7..0]** from 0 to 7 which is each index corresponds to each digit.
- **Cin** is a binary number to carry input.
- **Binvert** using to help in subtraction by inverting the input B.
- **OP[1..0]** The “Operation control” to control the circuit’s function.
  - OP = 00 do “AND” operation.
  - OP = 01 do “OR” operation.
  - OP = 10 do “Adder” operation.

For the outputs there are:

- **R[7..0]** 8-bit binary number output.
- **Cout**: binary number output to check if there is integer overflow of “Adder” circuit.

## Simulation

“AND” operation(OP = 00)

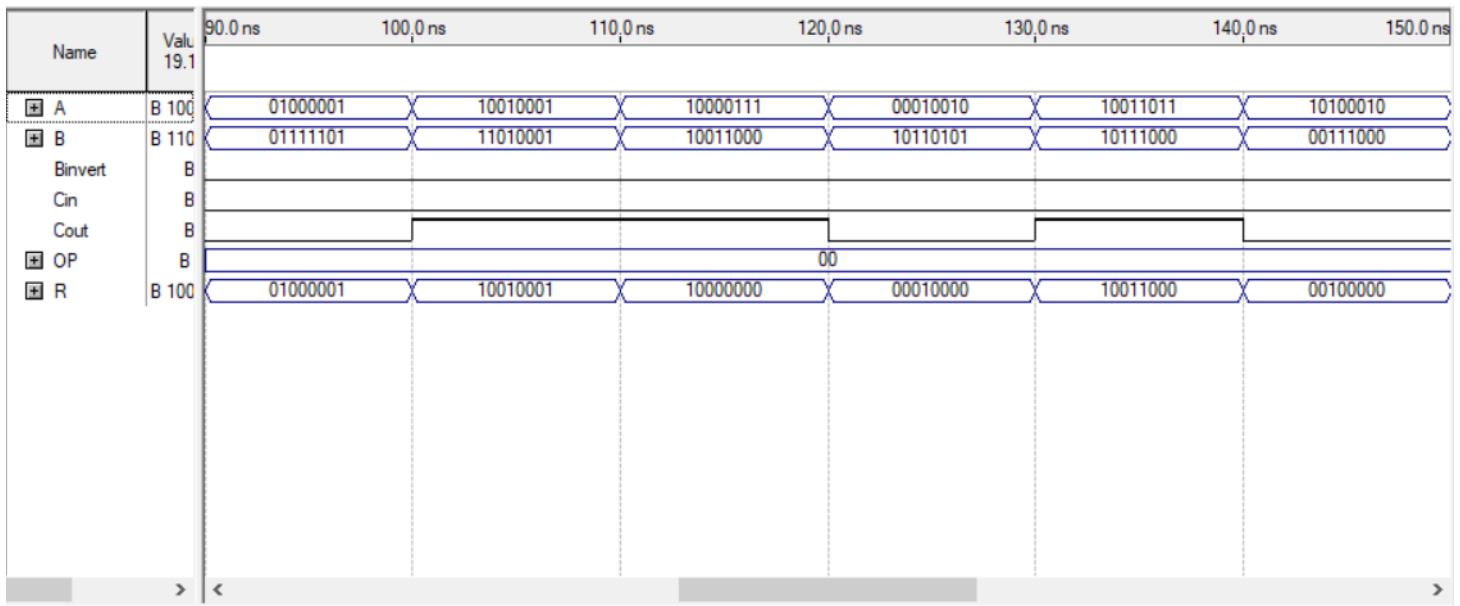


Figure 3: The result of “AND” operation simulation.

from the *Figure 4* shown, below as you can see if we compare each digit of the binary number of A and B for example

- 010000**1** and 0111110**1** the result(R) is 0100000**1**. We can say that the behavior is the same as the AND truth table in the **fourth** row.
- 01000**0**1 and 0111110**1** the result(R) is 010000**0**1. We can say that the behavior is the same as the AND truth table in the **first** row.
- 0100**0**01 and 0111110**1** the result(R) is 01000**0**01. We can say that the behavior is the same as the AND truth table in the **second** row.

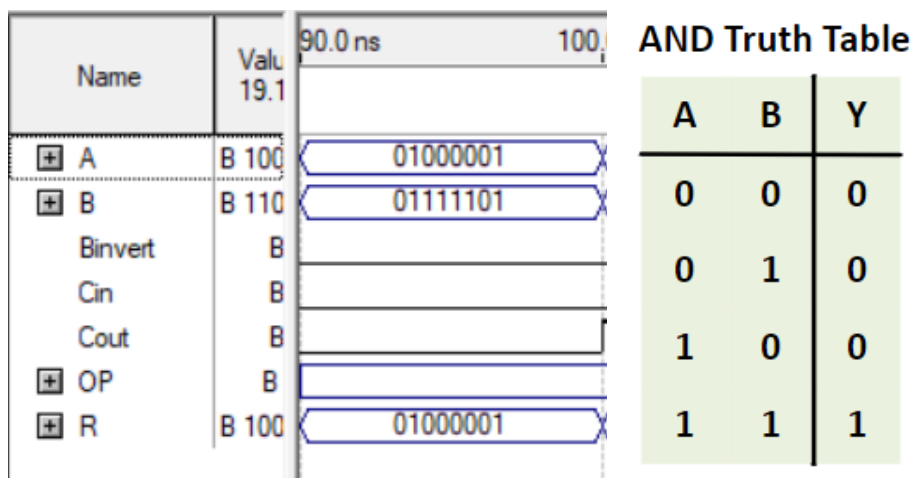


Figure 4: first section of 8-bit ALU and the “AND” truth table.

## “OR” operation(OP = 01)

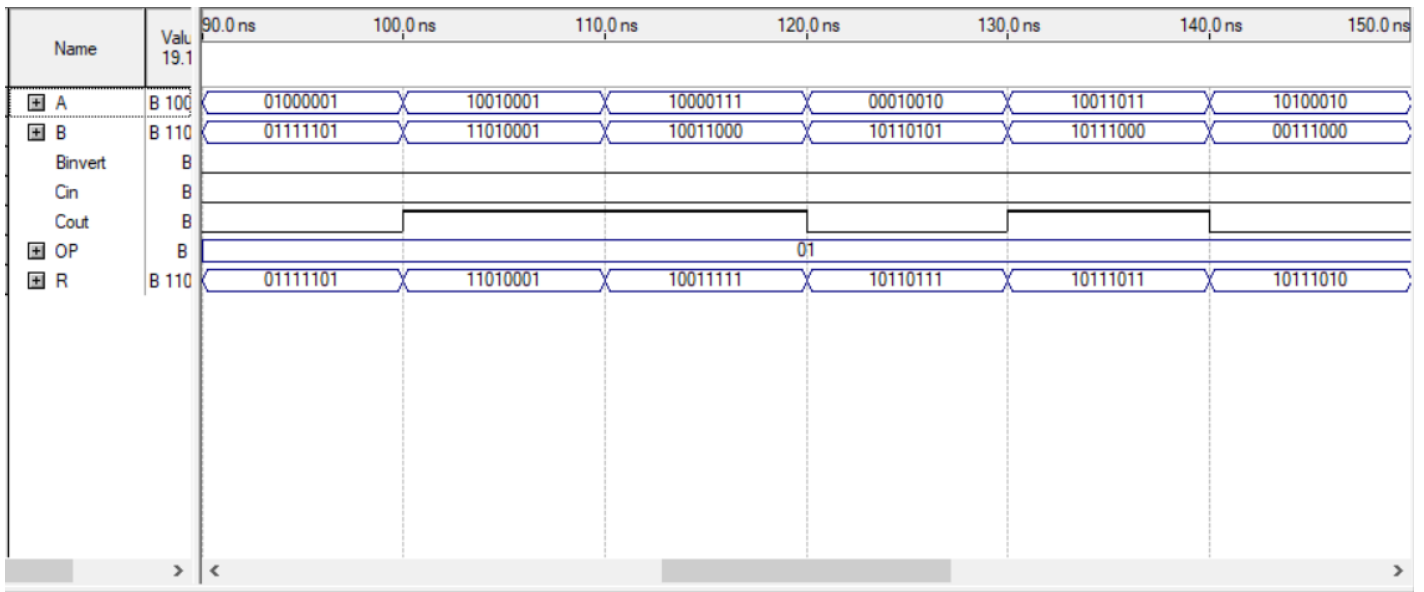


Figure 5: The result of “OR” operation simulation.

from the Figure 6 shown, below as you can see if we compare each digit of the binary number of A and B for example

- 010000**1** and 0111110**1** the result(R) is 0111110**1**. We can say that the behavior is the same as the AND truth table in the **fourth** row.
- 010000**1** and 011111**0**1 the result(R) is 011111**0**1. We can say that the behavior is the same as the AND truth table in the **first** row.
- 01000**0**1 and 01111**1**01 the result(R) is 01111**1**01. We can say that the behavior is the same as the AND truth table in the **second** row.

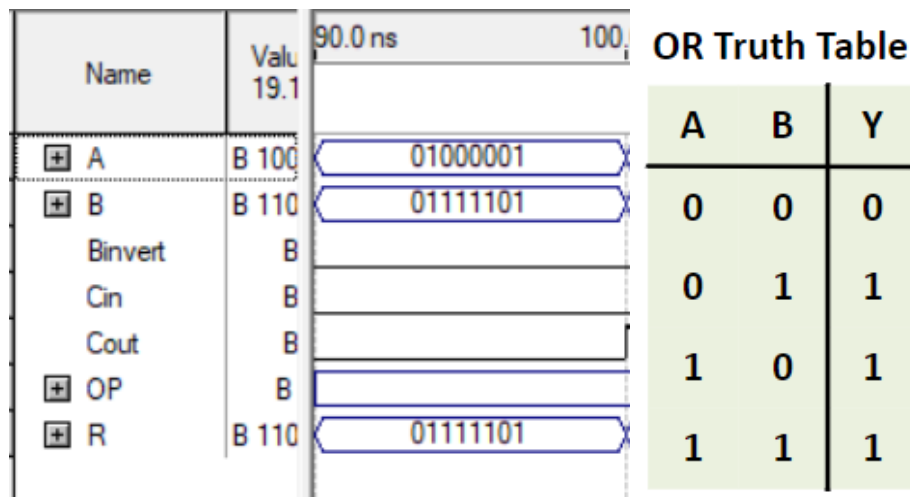


Figure 6: the first section of 8-bit ALU and the “OR” truth table.

## “Adder” operation(OP=10)

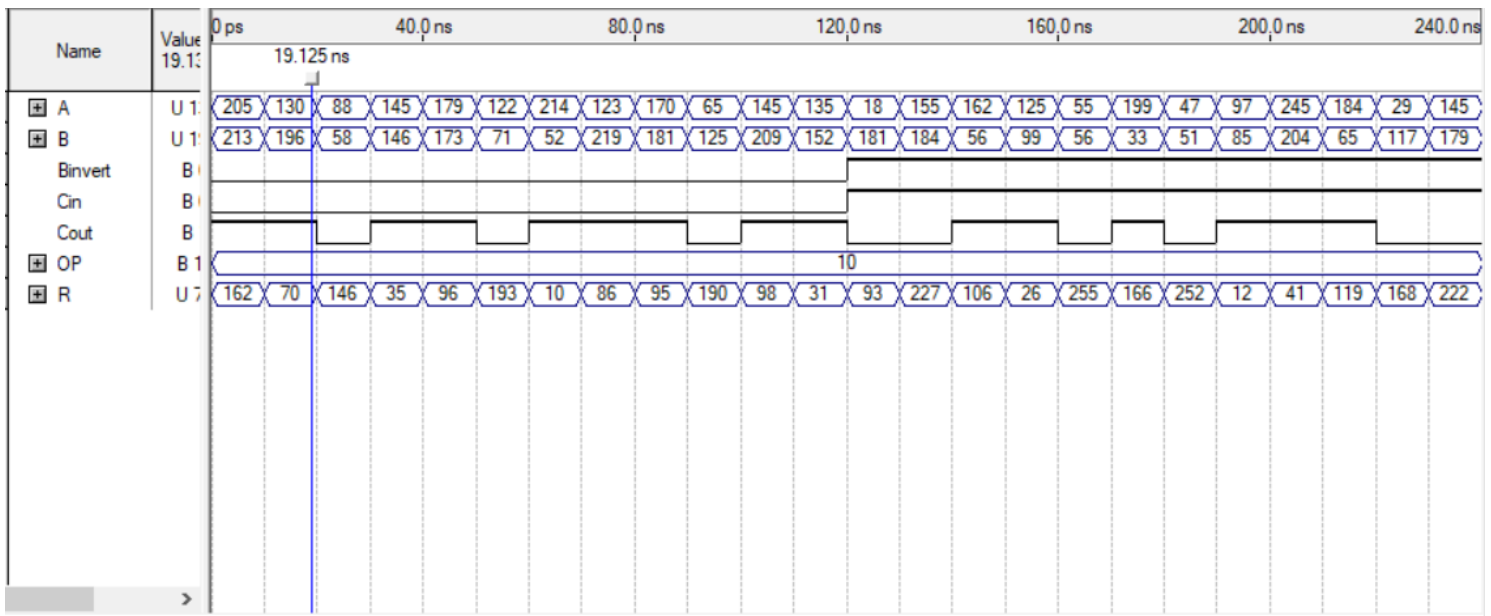


Figure 7: The result of “Adder” operation simulation.

For “Adder” operation is different from the other because there are two part which is ADD and SUB operation and this operation also work with Binvert, Cin, and Cout in this operation which the other part didn’t.

- **ADD part:**

Name	Value	0 ps
A	U 1:	205
B	U 1:	213
Binvert	B 1:	
Cin	B 1:	
Cout	B 1:	
OP	B 1:	
R	U 7:	162

Figure 8: ADD part example.

- Binvert is zero
- If Cout is present: There are some cases that the addition output will be integer overflow for example the first column:  $205 + 213 = 418$  but the limits of an 8-bit binary is 256. we can call this is integer overflow, then the result will start counting from zero again. We can subtracting the actual result(in this case) 418 minus 256 equal 162
- If Cout is zero: That means no integer overflow

- **SUB part:**

Name	Value	
	19.13	
<input checked="" type="checkbox"/> A	U 1:	162
<input checked="" type="checkbox"/> B	U 1:	56
Binvert	B 1:	
Cin	B 1:	
Cout	B 1:	
<input checked="" type="checkbox"/> OP	B 1:	
<input checked="" type="checkbox"/> R	U 7:	106

Figure 9: SUB part example.

- Binvert is present: because when we subtracting we can calculate by using the invert of B adding with A for example:  $162 - 56$ , the invert of 56 is  $(256 - 56) 200$  then,  $162 + 200 = 362$ .
- Cout is present: From the previous example as you can see 362 is integer overflow because it's over the limit, subtract  $362 - 256 = 106$  so the result is 106 as shown in the R column
- If Cout is zero: That means no integer overflow